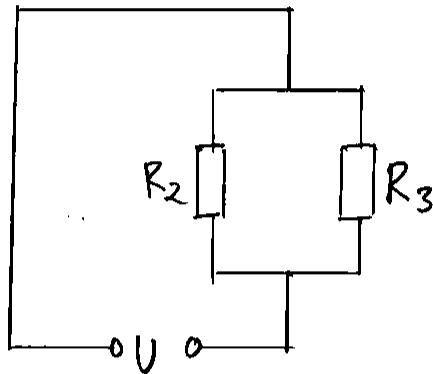


Musteraufgabe 6

3. Geg.: $R_2 = 176,3 \Omega$
 $P = 1100 \text{ W}$
 $U = 230 \text{ V}$

Schaltstufe 5:



$$R_{23} = \frac{U^2}{P} = \frac{230^2 \text{ V}^2}{1100 \text{ W}} = 48,09 \Omega$$

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{48,09 \Omega} = \frac{1}{176,3 \Omega} + \frac{1}{R_3}$$

$$\frac{1}{R_3} = \frac{1}{48,09 \Omega} - \frac{1}{176,3 \Omega} = 0,01512 \frac{1}{\Omega}$$

$$\Rightarrow \underline{\underline{R_3 = 66,12 \Omega}}$$